

Baluns, Ununs, and Related Topics

W7KVI, HARC Original: 3/26/16

This Presentation

- Informal & brisk 52 slides (too many unless you're an enthusiast!)
- Discussion encouraged if not extensive, interrupt me freely
- My motivation commercial, popular balun kit, inexpensive, insufficient instructions – installed on a 75m dipole, poor resulrs

Major Topics


- Why Baluns?
- Applications
- Types of Baluns
- Examples

Why & Where?

- Why do we need baluns and ununs?
 - Prevent current on outside of coaxial cable shield, which causes radiation pattern distortion
 - Due to Skin Effect
 - Convert impedances
 - Reduce need for, or demand on, antenna tuner
 - Prevent transmitter "foldback" at ~2:1 SWR
- Typical applications
 - Connect balanced and unbalanced structures Dipole to coax
 - Balanced feedline to coax
 - Use antenna on non-resonant frequencies

Skin Effect

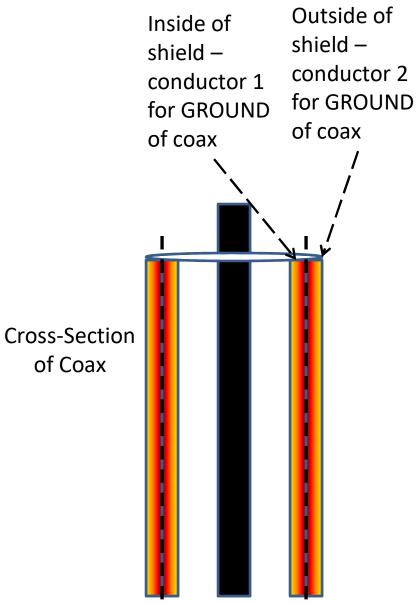- Property of AC current to flow mostly near the surface of a conductor
 - Skin Depth thickness containing 63% of current
 - At 10 MHz, skin depth = 21 μ m, or 0.000021m
 - Coax shield thick enough that it actually represents 2 separate conductors – inside and outside of shield
- Allows using pipes or tubes to reduce conductor cost



Unbalanced Coax connected to Balanced Antenna

- REASON #1 for BALUNS...
- Current from coax shield to dipole conductor (or reverse) has available 2 paths – inside and outside of coax shield.
- Now have current on OUTSIDE of coax – undesired!
- Feedline now radiates and is part of antenna – changes the radiation pattern, may place RF in the shack when touching "ground."

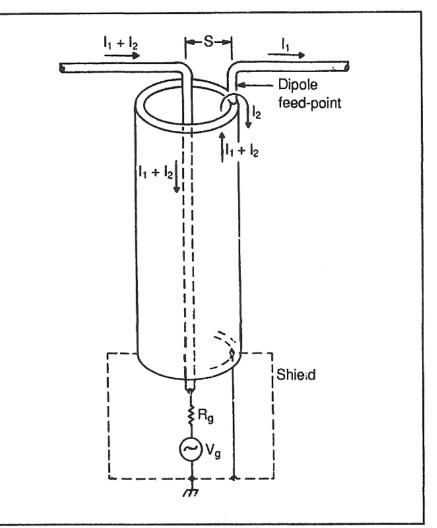


Figure 7-1. An illustration of the various currents at the feedpoint of a dipole. I_1 is the dipole current and I_2 , the inverted L (imbalance) current.

Why Impedance Transformation?


- REASON #2 for BALUNS...
- Antennas aren't usually 50 or 72 ohms, even though theory (properly) states a dipole is 72 ohms (only in free space, far from earth).
- Antenna impedances are highly dependent on proximity of the earth, and other objects such as trees and buildings.

Antenna Impedance Examples




First, How to Read Analyzer Data

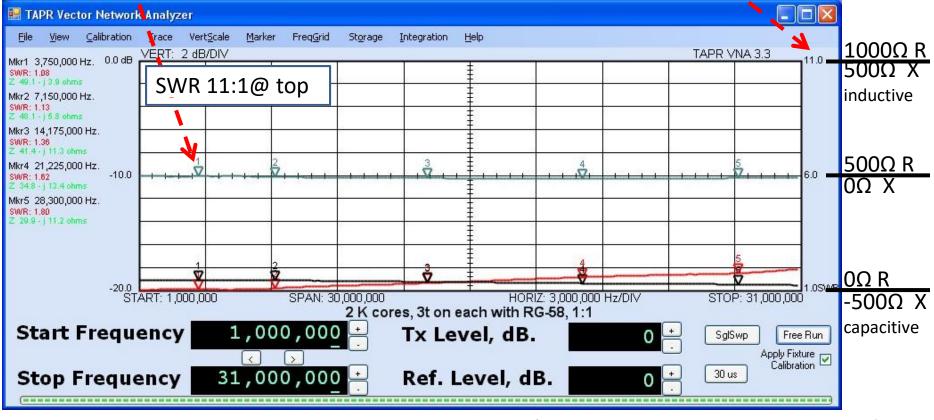- Typical traces SWR (red), R (black), X (gray)
 - SWR scale at right 1:1 to 11:1 or 1:1 to 3:1
 - X and R plotted 100 ohms/div, X centered (10 ohms/div in some plots)
- Markers in 160/80-10m ham bands





Baluns W7KVI 03/16

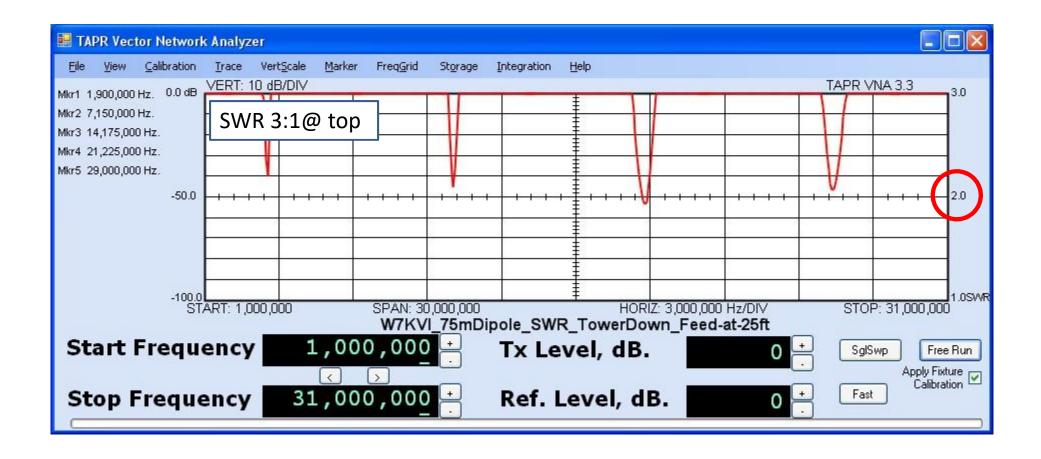Antenna Sweep – 75 m Dipole, tower down SWR (only) plotted on 3:1 max scale



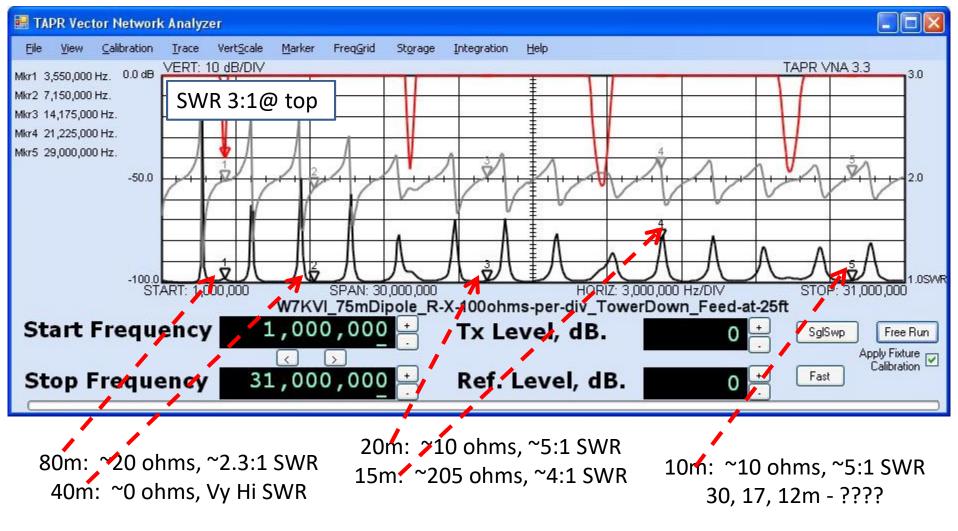
Antenna Sweep – 75 m Dipole, tower down R&X plotted at ± 100 ohms/div



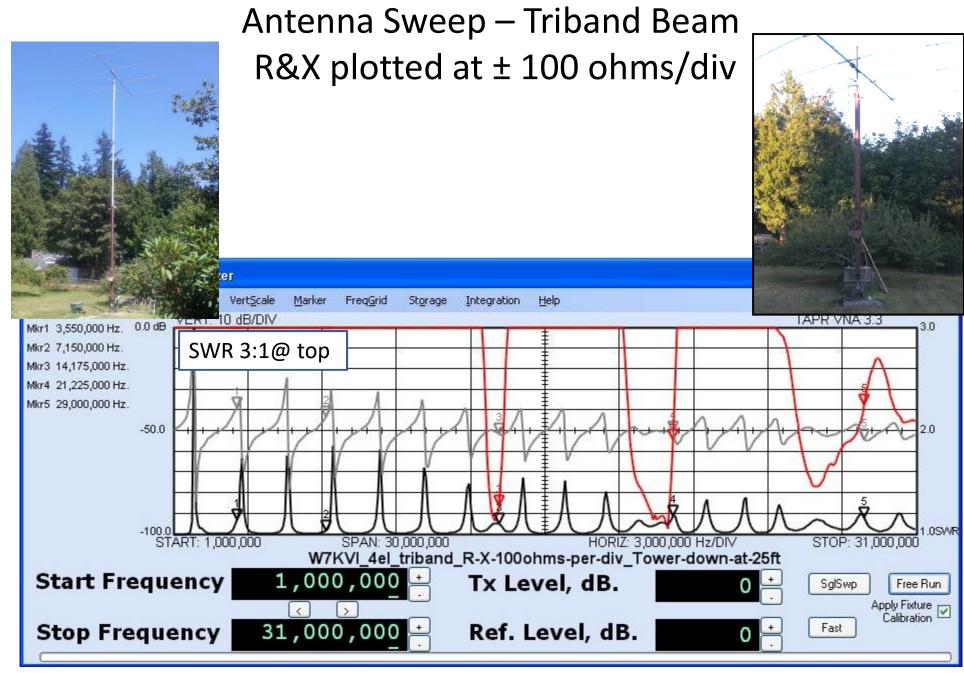

Baluns W7KVI 03/16


Antenna Sweep – Eaves Loop

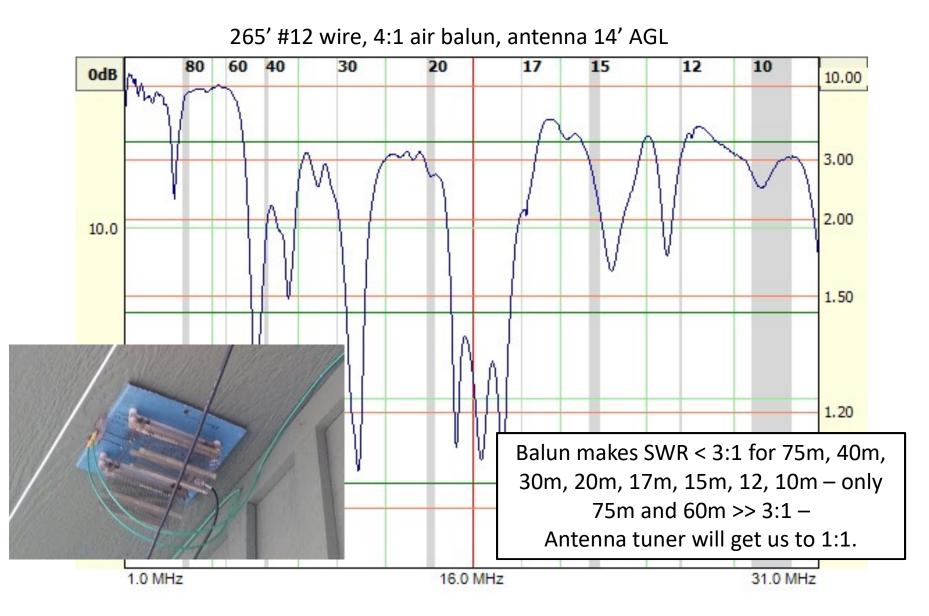

Antenna Sweep – 97' FlatTop

450 ohm ladder line, 4:1 air balun, 20' AGL, center on roof (temp) 60 40 20 17 15 12 30 10 80 0dB 10.00 3.00 2.00 10.0 SWR < 3:1 only for 60m! Much better 1.50 antenna tuner required, or diff balun Z ratio. 20.0 1.20 1.10 30.0 1.0 MHz 16.0 MHz 31.0 MHz

Fan (Multi-band) Dipole, 12' AGL

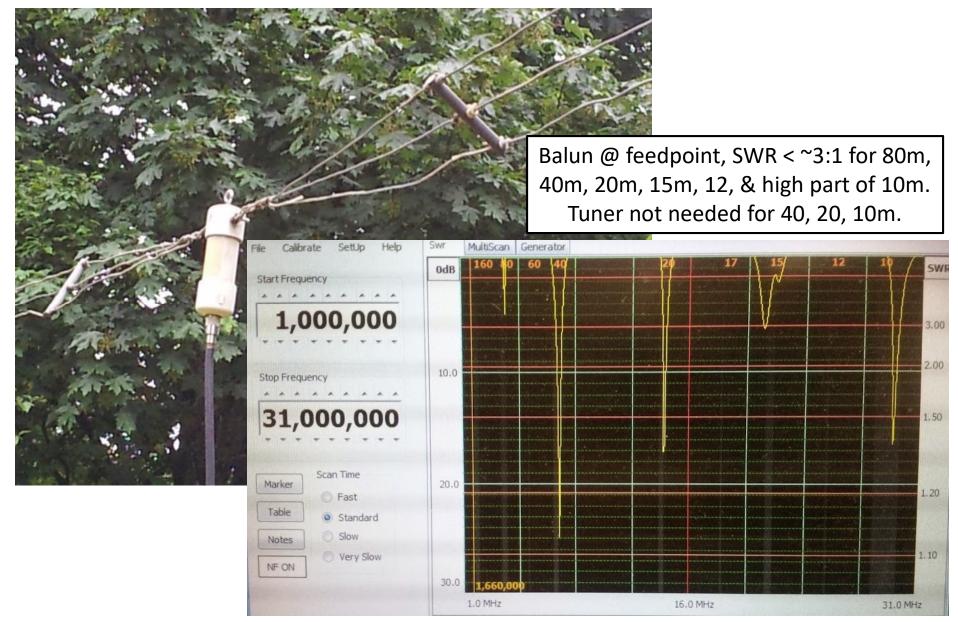

Baluns W7KVI 03/16

Types of Baluns and Ununs


- Choke (coiled feedline)
 - Merely an additional length of feedline
 - Presents high Z to current on outside of coax shield
- Flux-coupled (via a core material, incl air)
 - Relies on coupling between windings by flux in a metallic or ferrite core [typ. Ruthroff or voltage balun]
- Transmission-line (wound on a core material)
 - Uses parallel or coaxial transmission line, wound on a ferrite for choking action [Guanella or current balun]

Choke Balun (1:1)



Choke Unun

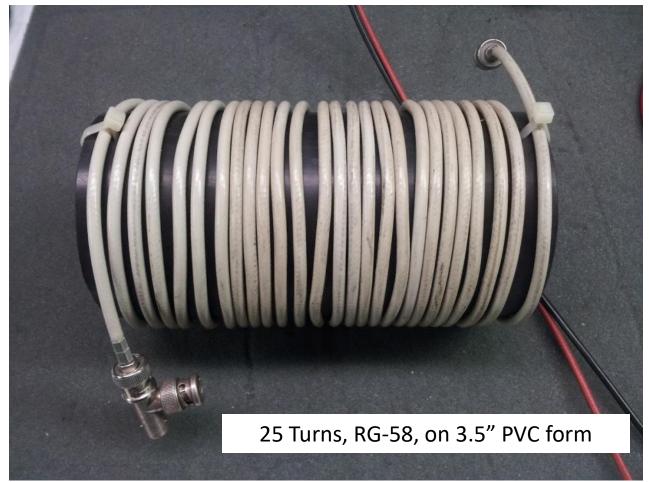Inserted in existing coaxial line, coil provides an inductive reactance to resist flow of common-mode currents (e.g., power line noise) on outside of shield – Unbalanced to Unbalanced



Choking Action








- Measure Z from shield to shield, 2' RG-58
- Several ferrite materials
 - Mix 31 beads
 - 3t, 2 beads → 1700 Ω
 - 1t, 4 beads → 350 Ω
 - Large Mix 43 toroids
 - 2t, 4 cores → 825 Ω
 - For connectorized cables

Choking Results

measure Z of the shield,						
men aud various remite	es over the coax to increase the Z of the shield Z, ohms, of shield on coax					
Config	2 MHz	3.7 MHz	7.1 Mhz	16.1 MHz	29.6 MHz	-
No Ferrite	10	15	30	72	150	
1t on K core	12	23	42	90	180	
2t on K core	22	44	86	163	370	
3t on K core	40	80	160	310	<mark>540</mark>	
1t on 4 ea K cores	26	50	105	250	420	
2t on 4 ea K cores	83	160	<mark>410</mark>	970	<mark>340</mark>	
4t on 3 ea K cores	240	520	>1K	730	310	Good choice for
1t on 4 ea Mix 31 beads	270	380	480	590	350	low HF band noise
2t on 4 ea Mix 31 bead	1240	1575	1290	580	285	>
1t on 8 ea Mix 31 beads	560	815	950	690	330	
1t on 4 ea Mix 43 cores	62	95	140	270	440	
2t on 4 ea mix 43 cores	230	360	575	822	368	

Flux-coupled and Transmission Line Baluns (Voltage and Current Baluns)

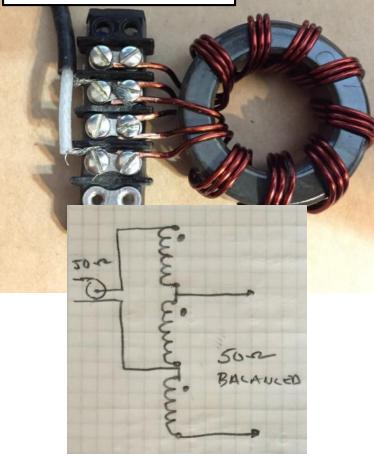Autoformer, not a parallel transmission line – Ruthroff balun (voltage)





One or more parallel transmission lines, connected various ways – Guanella balun (current) – core is used solely for choking action

Air Core Balun

- Classic balun using Airdux material
- 2 conductors in each coil, adjacent turns are different conductors!
- Configurable for 1:1 and 4:1



Classic Air-Core Balun - Application

OSCILLATORS

TOLL FREE 800-327-1282

- Convert parallel feedline to coax
- Types of Parallel Line
 - Open Feeder or Ladder' line
 - Typ 450 and 600 ohm
 - Twin Lead
 - Common for (old) outdoor TV antennas
 - Window line
 - Commonly available today



How Well Does it Work (4:1 Air-Core)?

- 300 Ω load →
 s.b. 75 Ω input,
 1.5 SWR, zero X
- Looks great except for resonance @ ~ 17 MHz





How Well Does it Work (4:1 Air-Core) @ a Lower Impedance?

- 220 Ω load →
 s.b. 55 Ω input,
 1.1 SWR, zero X
- Looks OK, lines not as flat, but resonance now larger



How Well Does it Work (4:1 Air-Core) @ a Still-Lower Impedance?

150 Ω load →
 s.b. 37.5 Ω
 input, 1.33
 SWR, zero X

 Large resonance effects We see that baluns (at least this one) have a DESIGN IMPEDANCE at which they work best – for this air core balun, it's $300/75 \Omega$ or higher – this makes sense, since 300 and 450Ω lines were common in tube-type equipment days.




Some Commercial Baluns

- Mixture of choke, ferrite, and air-core baluns
- Some 1:1, others 4:1
- <u>Caution</u> the specific examples in most cases are used baluns, with unknown service – these may not be representative of new examples.
- In some cases, corrosion had to be removed to obtain the results shown.

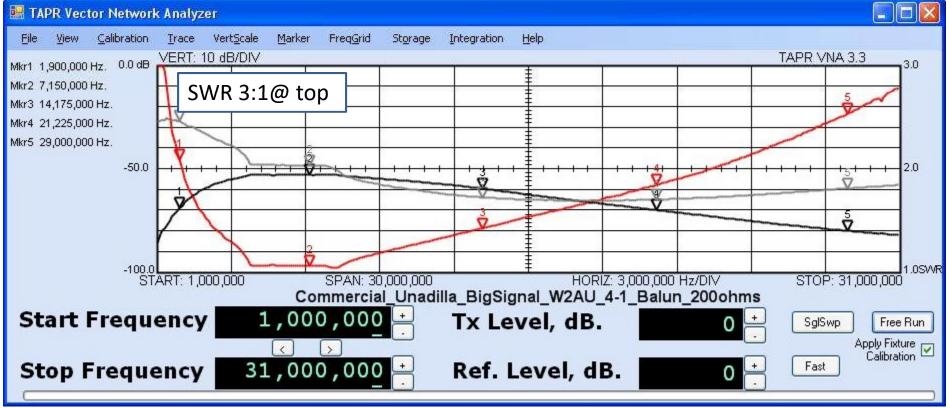
- 4:1 Not great!
- 2.5:1 @ 10m &
 1.8:1 @ 15m






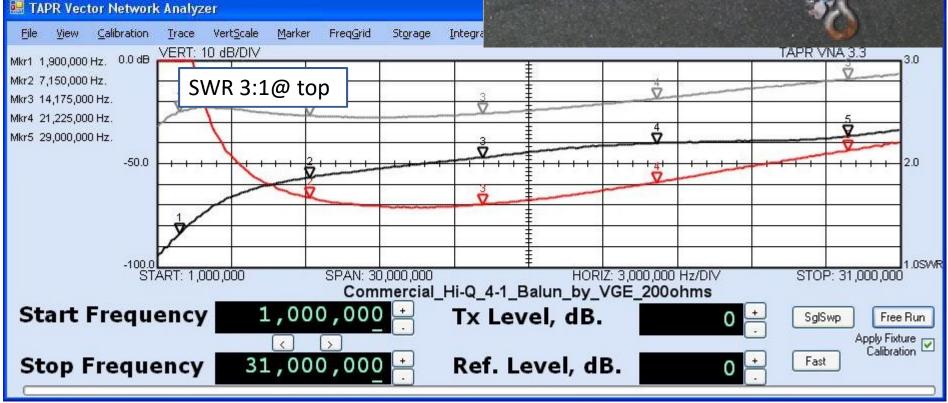
- 4:1 Not great!
- 1.6:1 @ 40,20m & 2.1:1 @ 10m





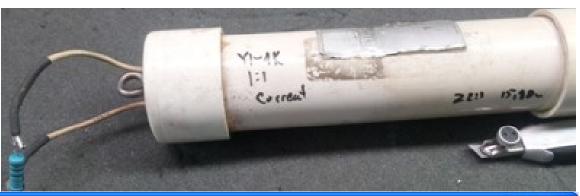
- 1:1 Not great!
- 2.1:1 @ 10m &
 1.8:1 @ 15m



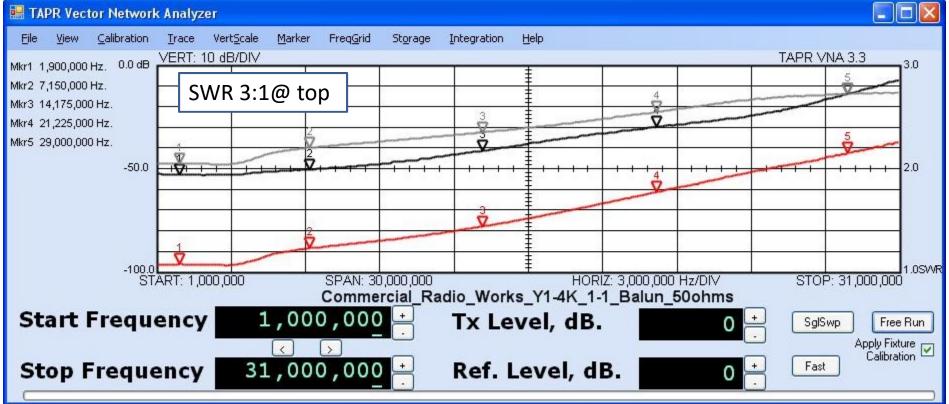

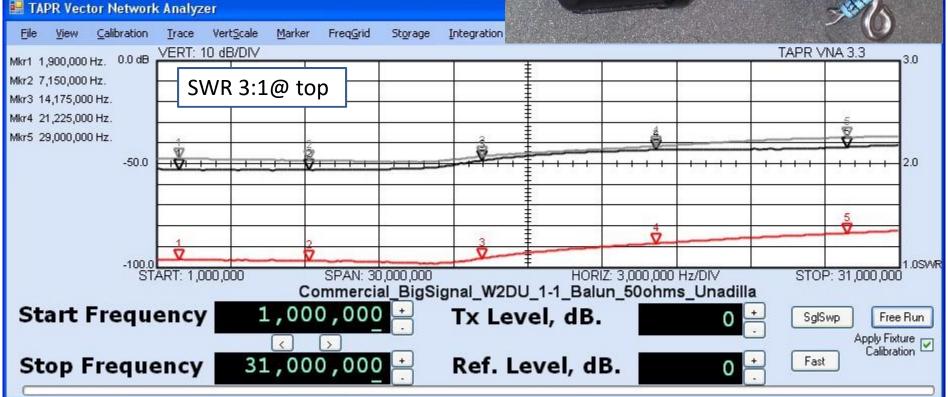
- 1:1, Much Better!
- 1.4:1 @ 10m &
 1.2:1 @ 15m






Commercial Balun #5, Unknown Source

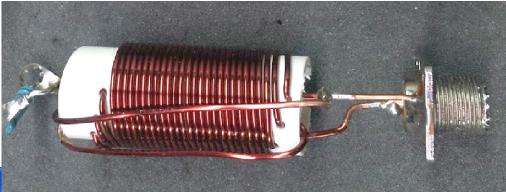- 1:1, Best so Far!
- ~1.7:1 @ 80m, but
 ~1.3:1 through 10m!



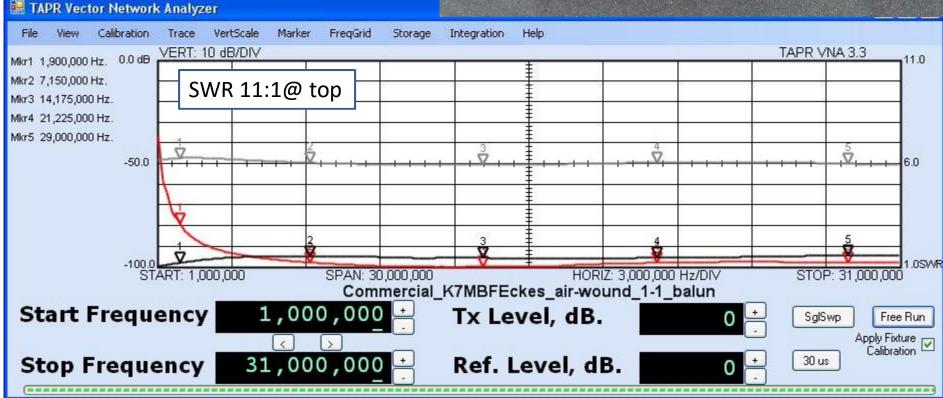

Home-Brew Examples

- Ruthroff (voltage) baluns rely on flux in a ferrite
- Guanella (current) baluns transmission lines, nearly zero flux, on a ferrite which is used to provide a choking impedance to shield currents

My Resources

- <u>Understanding, Building, and Using Baluns</u> <u>and Ununs</u>, Theory & Practical Designs, by Jerry Sevick, W2FMI, CQ Communications, Inc
- <u>Transmission Line Transformers</u>, by Jerry Sevick, W7FMI, Noble Publishing, Atlanta


My Materials (mostly per Sevick)

- Cores/Beads
 - T-200-2 (perm μ 10), powdered iron, large dia, part of \$6 kit
 - K (perm μ 290), NiZn ferrite,
 - 1.25" \$1.75
 - 1.5" \$7.00
 - 2" \$11.50
 - Mix 43 (perm μ 800), NiZn ferrite,
 - 13/8" \$1.52
 - 23/8" \$3.94
 - Mix 31 (perm μ 1500), MnZn bead
 - \$1.69

- Wire & Tape
 - #14 Copper wire, Imideze insulation
 - #16 Copper wire, enamel insulation
 - #18 Hookup wire (stranded)
 - Scotch 27 Glass electrical tape, maintain parallel lines
 - 3M Polyimide Type 97 tape, provide desired line impedance

Ruthroff (voltage) Baluns/Ununs

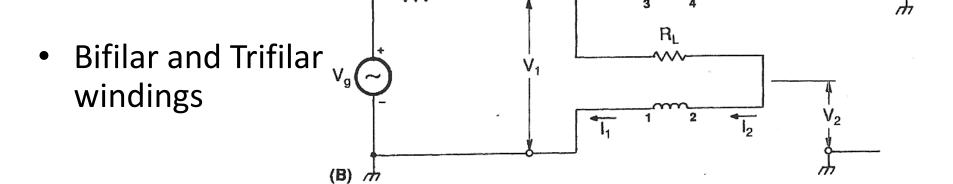
- Rely on flux in the core to couple between windings
- Generally add delayed to direct signals (4:1 shown)
- More susceptible to saturation (harmonics) and overheating $R_{a} = \frac{I_1 + I_2}{R_{a}} = \frac{I_1 + I_2}{I_1} = \frac{I_2}{I_2}$




Commercial Kit, Ruthroff 1:1 Balun

- T-200-2 core (μ 10), bifilar, flux-coupled
- Poor performance 20m (1.8:1) & above

Harring TAPR Vector Network Analyzer

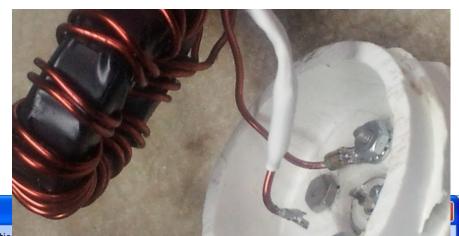


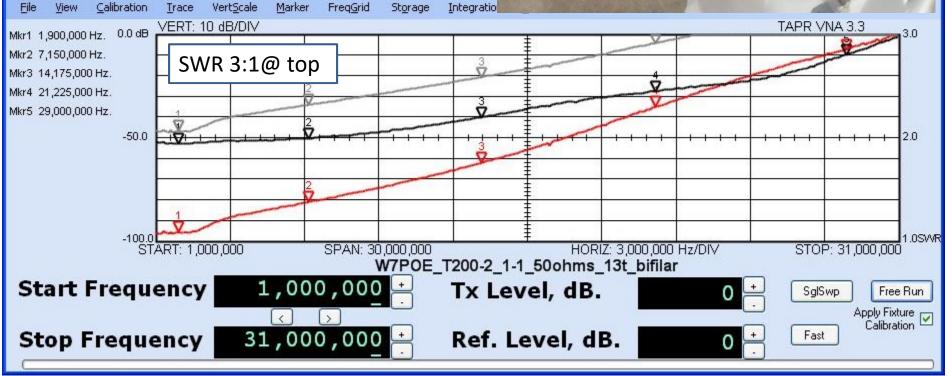

Commercial Kit, 2nd ver Ruthroff 1:1 Balun


T-200-2 core (μ 10), Trifilar, flux-۲ coupled, 7 turns

File

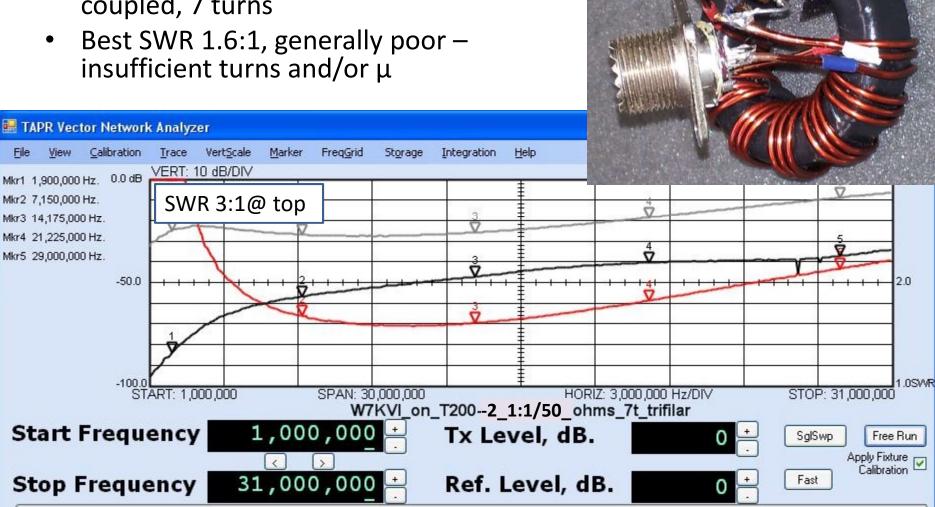


Commercial Kit, Ruthroff 4:1 Balun

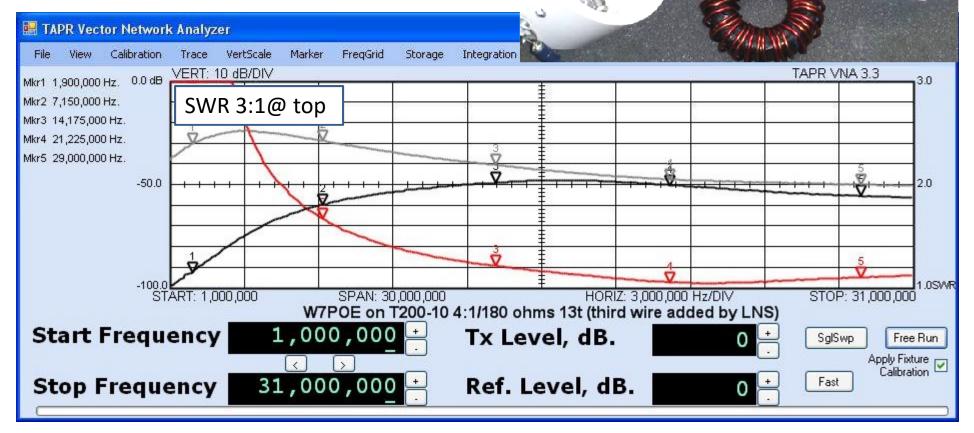- T-200-2 core (μ 10), Trifilar, flux-coupled, 13 turns
- Poor @ 3:1 80m, 1.7:1 40m, OK 20m & above



4:1 Ruthroff Balun

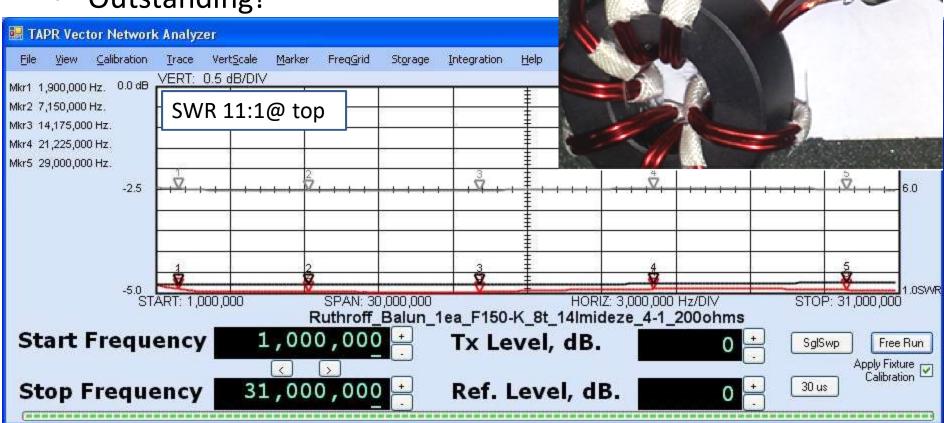
- 1.5" K core (μ 290), fluxcoupled, much better core
- Outstanding!



4:1 Ruthroff(Unun


200 ohing

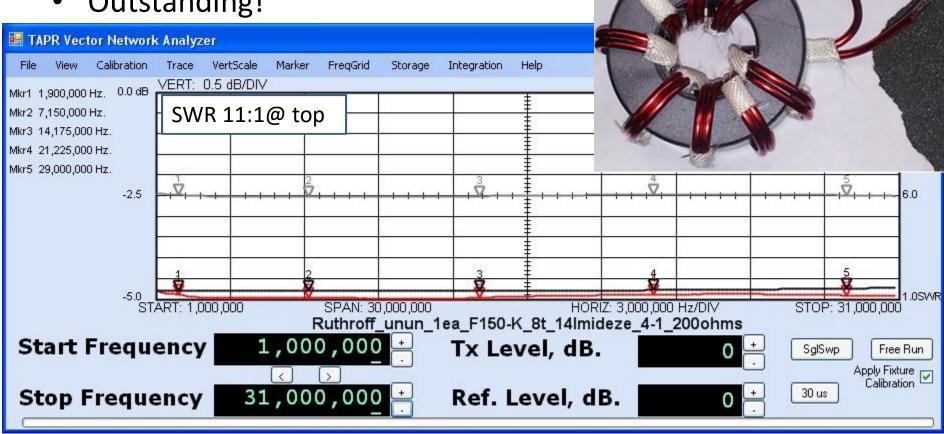- 1.5" K core (μ 290), flux-coupled, much better core
- **Outstanding!**




4:1 Ruthroff Balun, Large Mix 43 Core

- Mix 43 (μ 800)
- Nearly Outstanding!

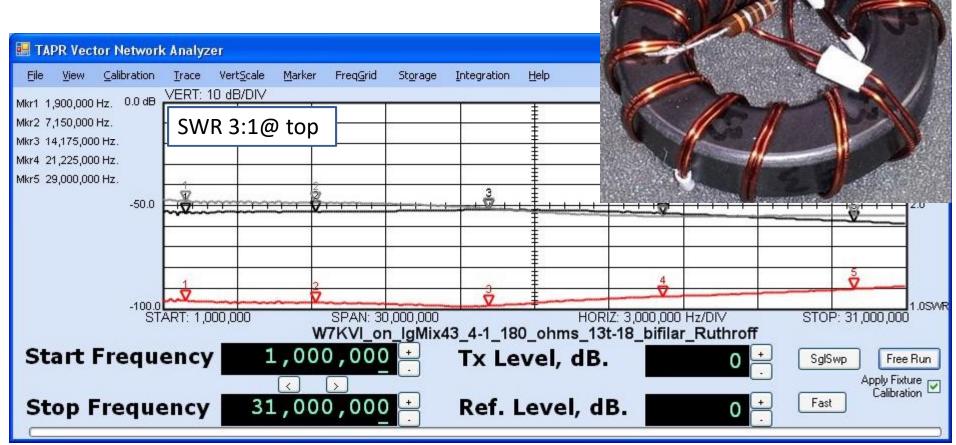


Guanella (current) Baluns/Ununs

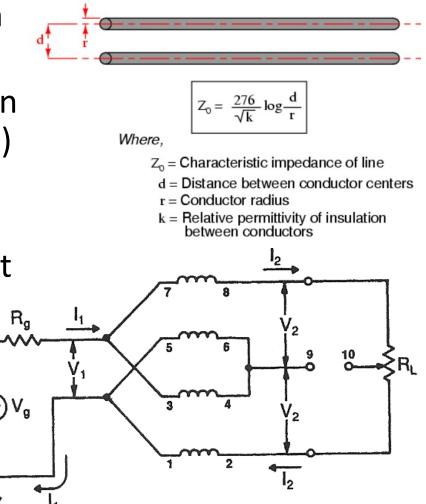- Rely on parallel transmission lines rather than flux in core
- As a result, very little concern about saturation (harmonics) and overheating
- Reasonably high μ core required to provide sufficient choking action
- Generally add inphase signals (4:1 shown)



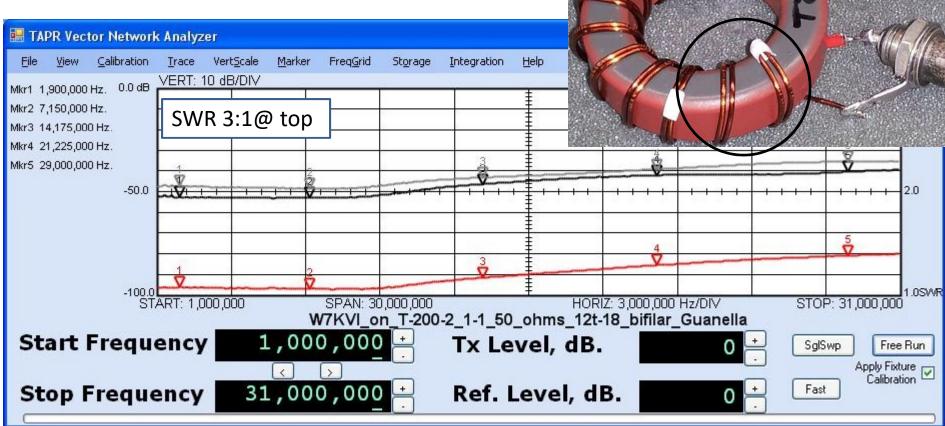
1:1 Guanella, T-200-2 core

- T-200 (μ 10), transmission line (no/low flux), spacing not well maintained
- Amazing for low perm core!
 1.4 SWR @ 10m
- Insufficient choking, due low μ



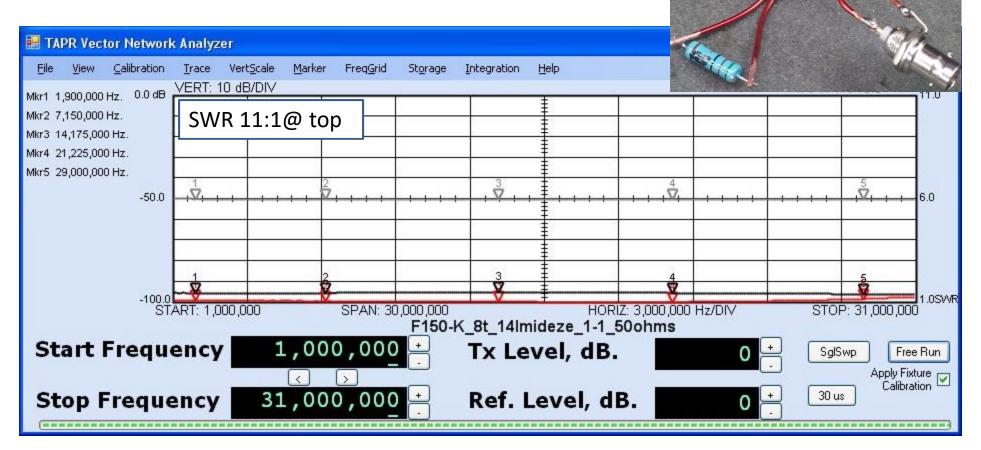1:1 Guanella, K core - #1 of 3

- Medium K core (μ 290), #14 wire, transmission line (no/low flux)
- Zline 25 ohms impedance very good (flat SWR, R, X)




1:1 Guanella, Back-back, loss measurement - #2 of 3

- 2 identical cores as previous slide for loss measurement
- Newblue trace on graphic loss for 2 cores at 0.5 dB per division
- @ 10m, ~0.1 dB loss per core or ~98% eff.!


🔜 TAPR Vector Network Analyzer



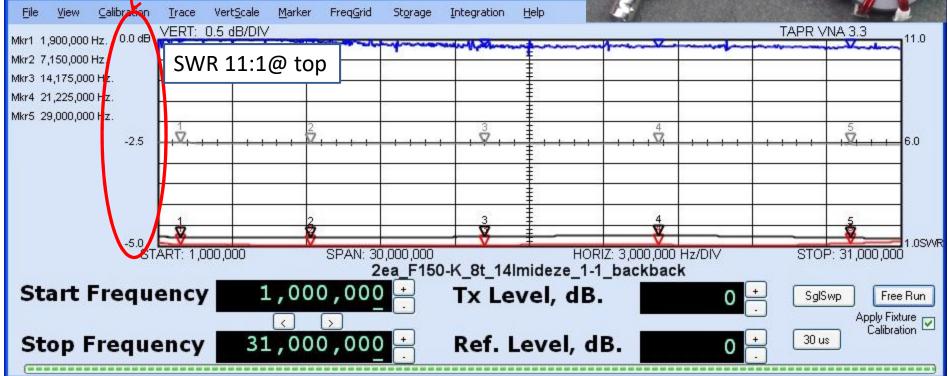

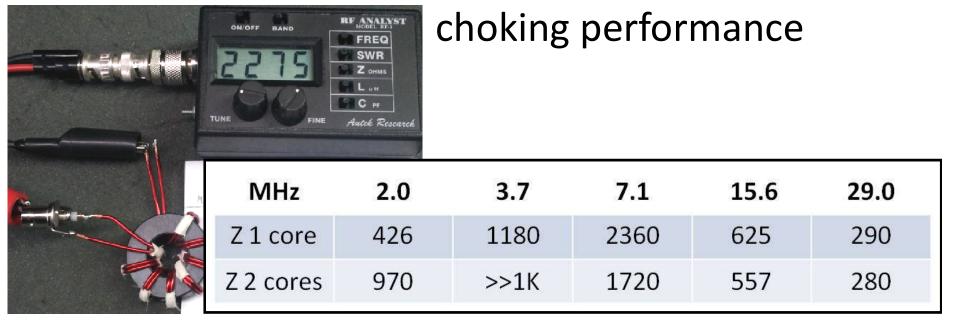1:1 Guanella, K core – Sufficient choking? #3 of 3


- Measure input shield to (balanced) output lead
- Z ≥ ~500' (10 times characteristic impedance) except for 10m, use more turns for better 10m



4:1 Guanella, 1st Effort - YUK


- Mix 43 core (μ 800), intended transmission line Z100

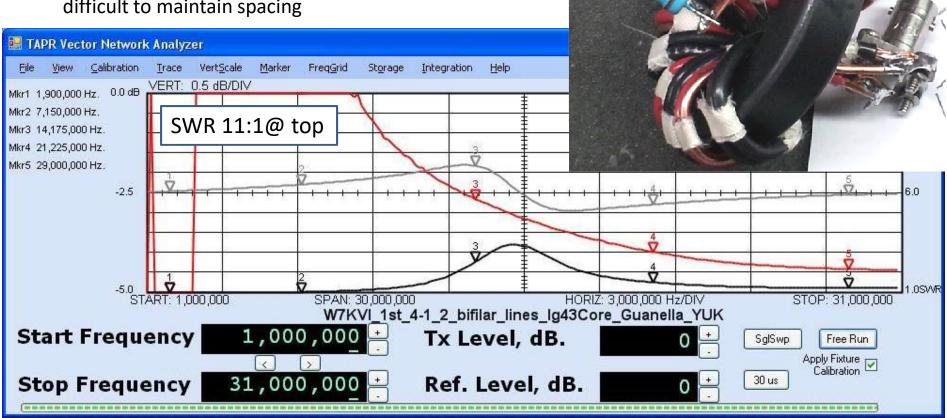 #12 house wiring, but one line solid, one stranded, removed one insulation to lower Z
- Something major wrong! Stranded wire too flexible difficult to maintain spacing



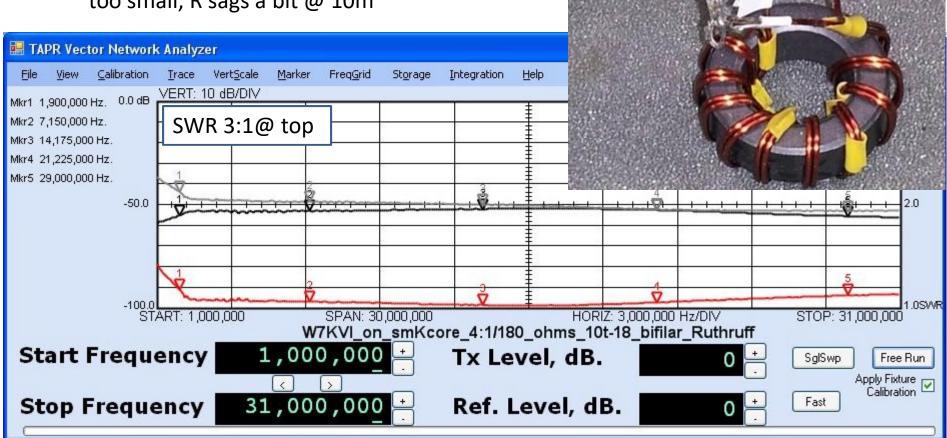
4:1 Guanella Balun, K core

- Medium K core (μ 290), transmission line Z100
- Nearly Outstanding! Wire dia a bit too small, R sags a bit @ 10m



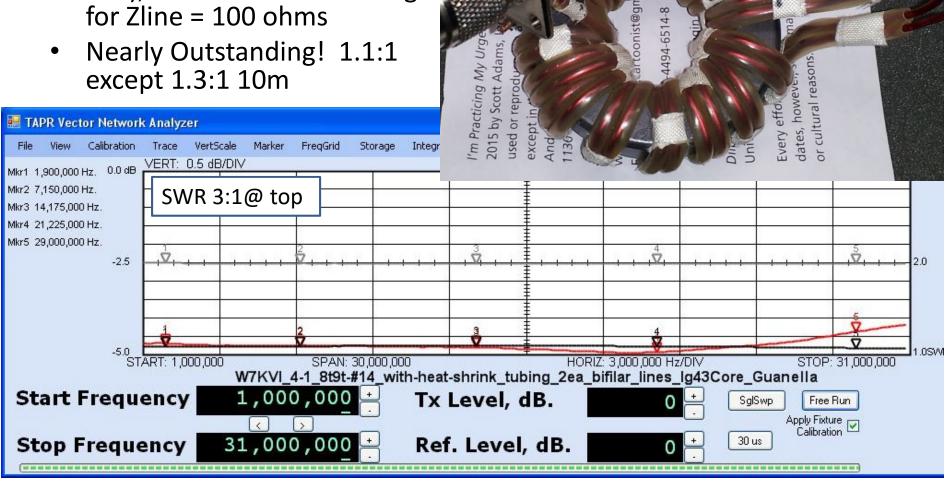4:1 Guanella, "High-power" Mix 43

 Large 43 (μ 800), transmission line (no/low flux), #14 wire with sleeving for Zline = 100 ohms




4:1 Guanella, "Low-Power"

- Smallest K (μ 290), transmission line (no/low flux), hookup wire
- 1.2:1 or better, 160-10m

🔜 TAPR Vector Network Analyzer

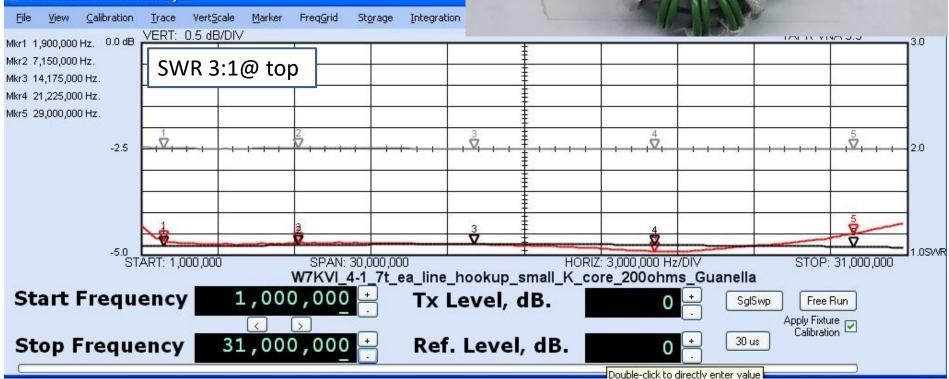- 100w continuous, 300w peak
- Very small, light, inexpensive





Some Conclusions

- Commercial baluns may have poor or mediocre performance testing required
- Ruthroff (voltage) baluns work well if core has sufficiently high permeability (well above 10!)
 - Flux-based, can be saturated (harmonic generation) and overheat
- Guanella (current, transmission line) baluns always worked well, even on low-perm cores
 - No/low flux, so saturation (harmonic generation!) and heating are likely not an issue
 - But....low-perm cores not likely to provide sufficient choking action
- Choosing the right core is key!
- Baluns are easy and inexpensive to make.

- Thanks for listening!
- Q & A, More Discussion
- Next Steps?
 - Balun-measuring session bring any baluns not in the air!
 - Balun-building session Interest?

- Thanks for listening!
- Q & A, More Discussion
- Next Steps?
 - Balun-measuring session bring any baluns not in the air!
 - Balun-building session Interest?